

Student ID:		Lab Section:	
Name:		Lab Group:	

Experiment No. 5

Study of I-V Characteristics of Linear Circuits & Verification of Thevenin's Theorem and Maximum Power Transfer Theorem Using Software (LTSpice) Simulation.

Part 1: Introduction to Simulation using LTSpice & Study of I-V Characteristics of Linear Circuits

Objective

The aim of this experiment is to introduce a circuit simulation software (LTSpice) and to acquaint students with the concept of I-V characteristics. They will simulate I-V characteristics of some circuits consisting of linear components using LTSpice.

Theory

I-V characteristics, also known as current-voltage characteristics, describe the relationship between the current flowing through a device/circuitry and the corresponding potential difference (voltage) across it. This concept is commonly used in the field of electronics and electrical engineering to analyze the behavior of various components such as resistors, diodes, transistors, and in general, circuits.

I-V characteristics provide a way to understand how current and voltage interact in electrical and electronic components and circuits. By analyzing these characteristics, circuits/devices can be designed and optimized, appropriate components can be selected, and the behavior of devices under different operating conditions can be predicted.

A circuit is linear if its I-V characteristic is linear, represented by a straight line in an I versus V plot. A circuit composed of linear components (resistors, voltage sources, current sources) has a straight line I-V characteristic.


For a simple resistor, the I-V characteristics follow Ohm's Law, which states that the current passing through a resistor is directly proportional to the voltage applied across it. Mathematically, this relationship can be expressed as $I = \frac{V}{R}$, where I is the current, V is the voltage, and R is the resistance. The characteristic line passes through the origin.

The I-V characteristic of an ideal voltage source (an ideal voltage source is a theoretical concept that maintains a constant voltage across its terminals, regardless of the current flowing through it.) is a vertical line on an I-V graph, indicating that the voltage remains constant (V) regardless of the current (I). Mathematically, it can be represented as $V = \text{constant}$. Real life voltage sources (for example, DC power supply in our labs) do not exactly behave this way, but should closely resemble an ideal voltage source. Similarly, an ideal current source has an I-V line parallel to the voltage axis since it supplies a constant current with theoretically any voltages across.


Procedures



Simulation using LTspice

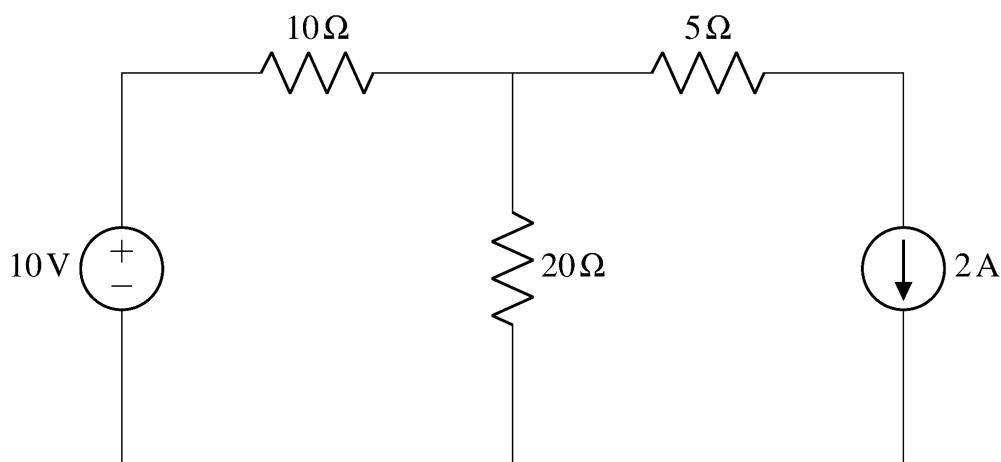
Let's get introduced to LTspice by simulating the simple circuit shown below (**Circuit 1**).



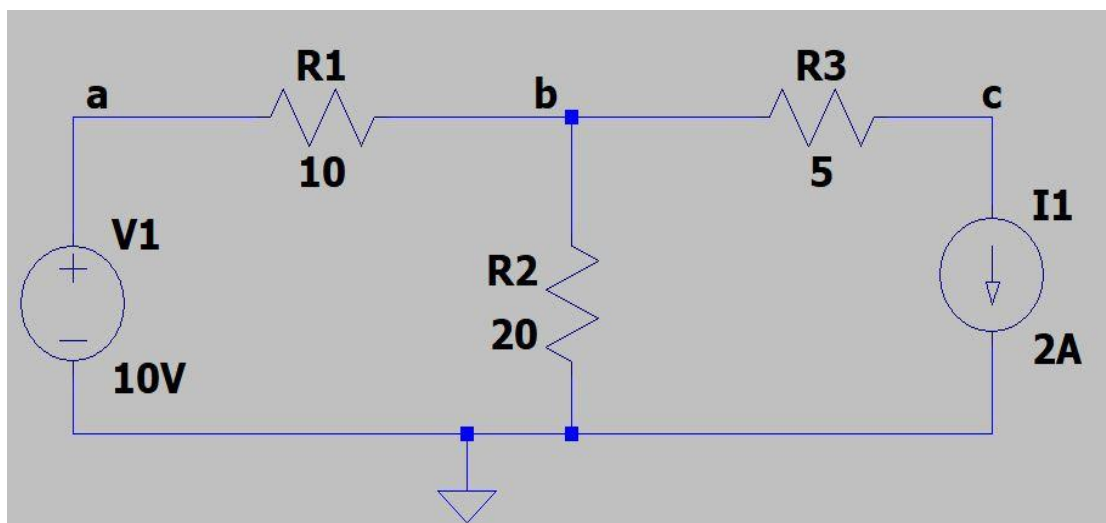
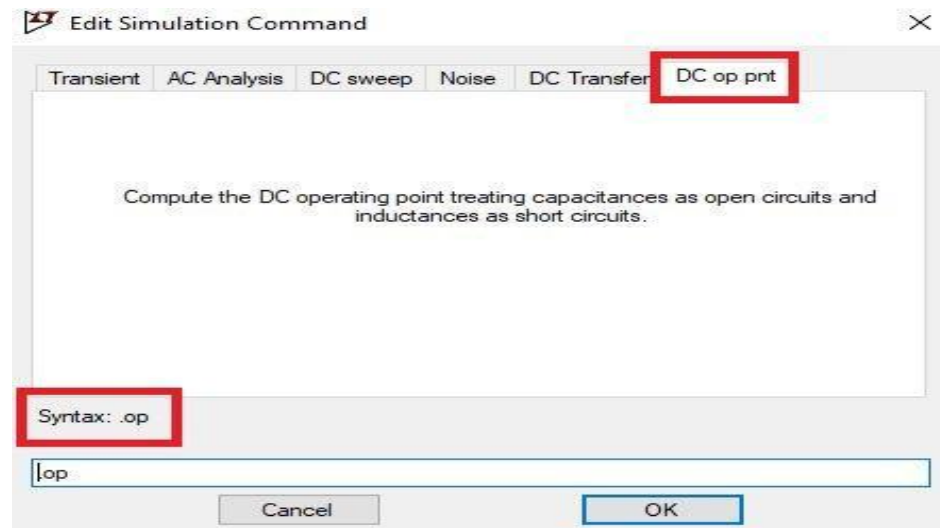
Circuit 1

- Open a new schematic window by clicking **File** → **New Schematic**. To find the required circuit components, **Right-click on blank space** → **Draft** → **Component** or click on the ‘**Component**’ icon  from the toolbar right above the schematic window. A window titled ‘**Select Component Symbol**’ will appear. Type the keyword for a component to be inserted. For example, for a resistor type ‘**resistor**’ → **select the component** → **click OK**. Press **CTRL + R** to rotate the component by 90° if necessary. **Left click** on any suitable place in the grey interface to place it. Press **ESC** to deselect the component. To assign the required value (Resistance, Voltage, Current etc.) to each component **Right click on the component symbol placed in the schematic** → **Fill up the corresponding box**.
- To connect the circuit components **Right-click on blank space** → **Draft** → **Draw Wire** or click on the ‘**Wire**’ icon from the toolbar.


- Find the ground symbol from the toolbar  , place it on the schematic and connect it to the circuit.
- Label the nodes of the circuit using '*Label Net*'. Find '*Label Net*' from the toolbar by clicking this  icon or *Right-click on blank space* → *Draft* → *Label Net*. After these, your circuit should look like this,




- To analyze the circuit (to get the node voltages and branch currents), we have to do '*DC operating point*' analysis.
To run the 'DC operating point analysis, we have to write the analysis command. First, find the '*Spice Directives*' option by *Right-clicking on the schematic* ☐ *Draft* ☐ *Spice Directives* or clicking on the "SPICE Directive"  icon from the toolbar .
- After clicking the '*Spice Directives*', the '*Edit Text on the Schematic*' window will appear. Now *Right-click on the blank space on this window* ☐ *Select 'Help me Edit'* ☐ *Analysis Command*. A window titled '*Edit Simulation Command*' will appear. Select '*DC op pnt*' ☐ *OK*. It will generate a '.op' command, which is the command for DC operating point analysis. Place this command somewhere in the schematic.




[Notice the ‘.op’ syntax for DC operating point analysis. You could just write the command in the command editor box and place that command in the schematic.]

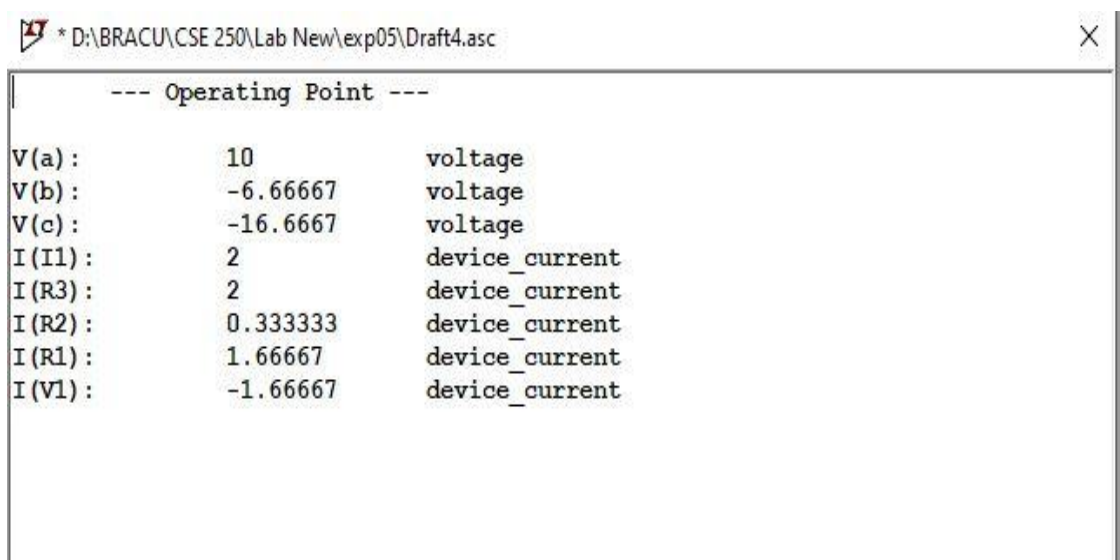- To run the simulation, click **‘Run’**. Find the **‘Run’** button  from the above toolbar or **Right-click on the schematic → Run**.
- After clicking ‘Run’ a new window titled **‘Operating Point’** will appear, containing all node voltages and branch currents.




I-V Characteristic plotting using LTspice

In **Experiment 4**, we assessed the IV characteristics graph of a given circuit and that of its equivalent circuit too and found that the IV graphs are exactly the same for both circuits, which confirms their equivalency. We can easily get the IV characteristics of those circuits using LTspice. Here are the circuits we studied in Experiment -04.

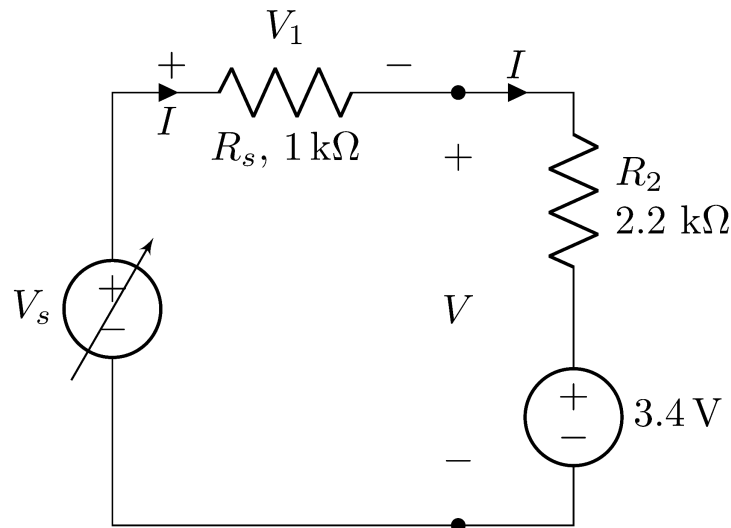


Circuit 2

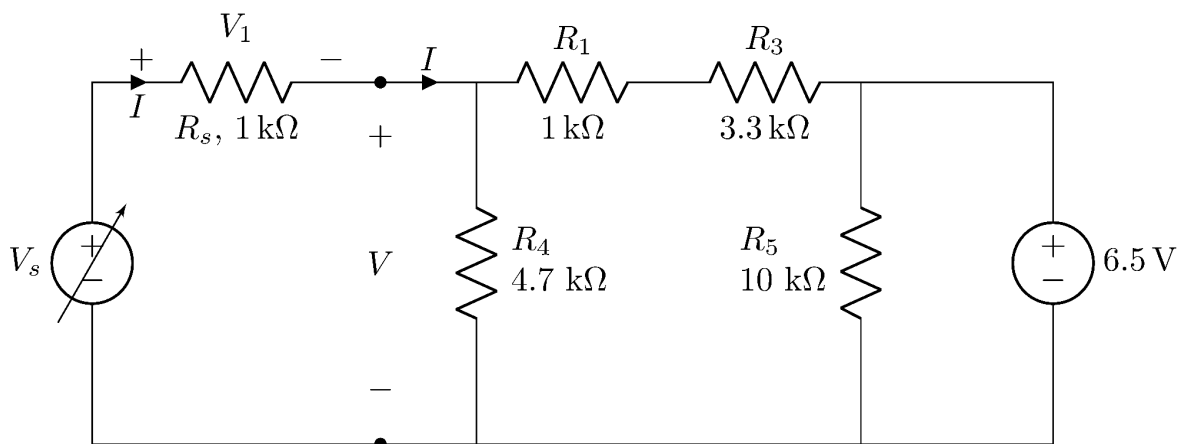


Circuit 3

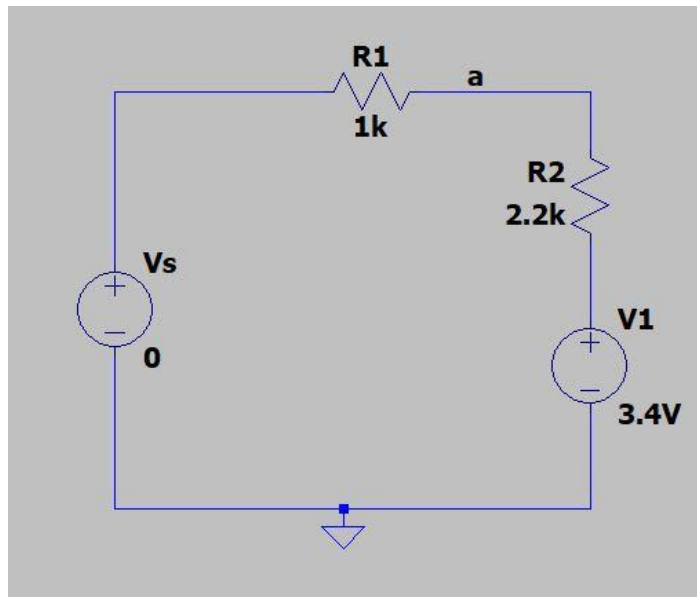- Draw **Circuit 2** shown in a new schematic in LTspice. Modify the components with their values and name the nodes. Label the nodes. For the variable voltage source ' V_s ' shown in the circuit, we will use a normal voltage source and vary its value during simulation.




Note that, here the variable voltage source has been renamed to 'Vs' and assigned with a value of **0 Volt**.

- To plot the IV characteristics graph, we need to vary the voltage of the source 'Vs'. And to do so, we have to do 'DC Sweep Analysis'. Now Find the '**Spice Directives**' option by **Right-clicking on the schematic** ☐ **Draft** ☐ **Spice Directives** or find it from the toolbar above.
- After clicking the '**Spice Directives**', the '**Edit Text on the Schematic**' window will appear. Now **Right-click on the blank space on this window** ☐ **Select 'Help me Edit'** ☐ **Analysis Command**. A window titled '**Edit Simulation Command**' will appear. Insert values in the boxes as below and click OK. It will generate a transient analysis command. Place the command somewhere on the schematic.

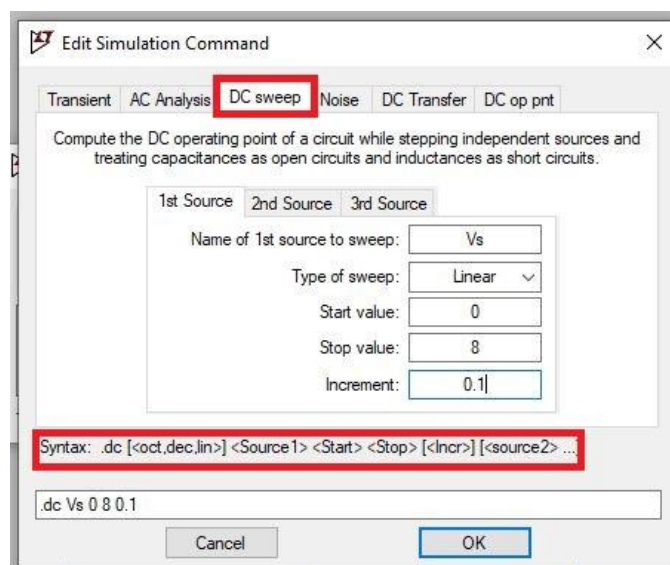


[Notice the '.dc' syntax for DC Sweep Analysis. You could just write the command in the command editor box and place that command in the schematic.]

- To run the simulation, click **'Run'**. Find the **'Run'** button from the above toolbar or **Right-click on the schematic → Run..**
- After the simulation 'run' is complete, a blank plot window will appear. Notice that in the X axis it shows the voltage of source 'Vs'. In the I-V characteristics graph, there should be voltage of the node 'a' (according to the circuit) in the X axis. To show the voltage of node 'a' in the X axis, **Right click on the X axis → Type V(a) in the 'Quantity plotted' box → OK.**

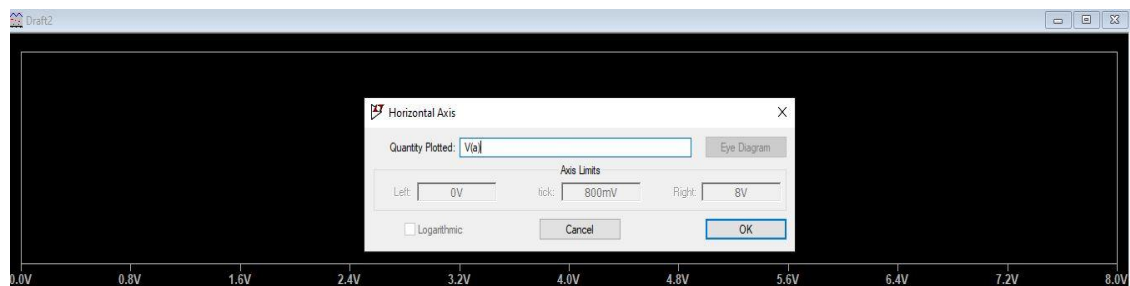

- To plot the current, **Right click on the blank space in the plot window → Add Traces.** A new window will appear. Select **I(R1)** (according to the circuit) and click **OK.**
- To extract data from a plot/response, use the **data cursor**. A cursor for a particular trace will appear by clicking on the name of that trace. The data point of the cursor can be moved by the arrow keys (navigation keys) on the keyboard.

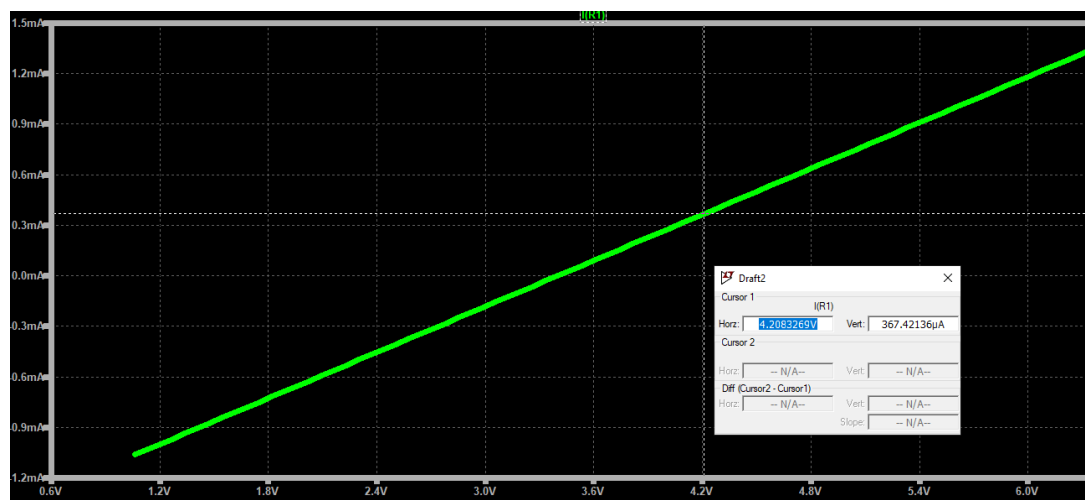

Lab Work: Simulate and plot the I-V characteristics of **Circuit 3** following the steps mentioned above. You should get the same result as you did in the hardware lab.

Part 2.1: Verification of Thevenin's Theorem using Software

Simulation (LTSpice)

Objective

The aim of this experiment is to verify Thevenin's theorem with reference to a given circuit using LTSpice. They will find out the Thevenin's equivalent circuit parameters (V_{OC} , I_{SC} , R_{th}) of a given circuit using simulation and determine the Thevenin's equivalent circuit. They will also simulate I-V characteristics of the given circuit and its Thevenin's equivalent circuit using LTSpice to verify Thevenin's theorem.


Theory

It is often desirable in circuit analysis to study the effect of changing a particular branch element while all other branches and all the sources in the circuit remain unchanged. Thevenin's theorem is a technique to this end, and it greatly reduces the number of computations that we have to do each time a change is made. Using Thevenin's theorem the given circuit except the particular branch to be studied is reduced to the simplest equivalent circuit possible and then the branch to be changed is connected across the equivalent circuit.


Thevenin's theorem states that any two-terminal linear bilateral networks containing sources and passive elements can be replaced by an equivalent circuit consisting of a voltage source (V_{th}) in series with a resistor (R_{th}), where,

V_{th} = The open circuit voltage (V_{OC}) at the two terminals A & B.

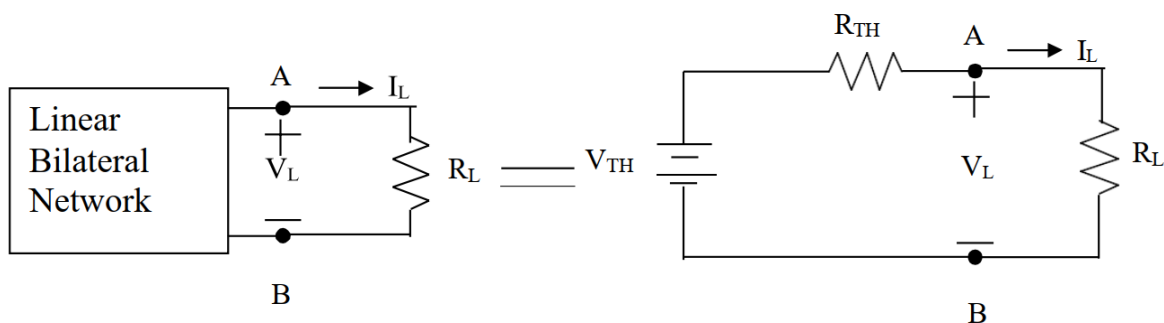R_{th} = The resistance looking into terminals A and B of the network with all sources removed.




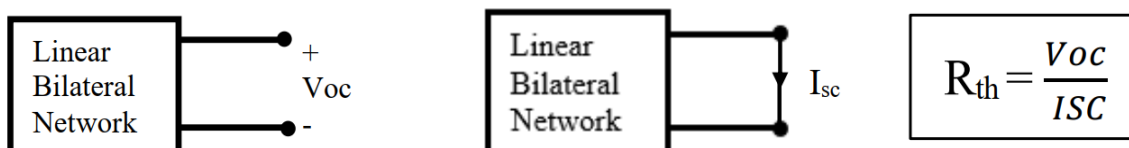There are several methods for determining Thevenin resistance R_{th} . An attractive method for determining R_{th} is: (1) determine the open circuit voltage, and (2) determine the short circuit current I_{SC} as shown in the figure; then



Methodology of Determining Thevenin's Circuit Parameters (V_{OC} , I_{SC} , R_{th})


In this experiment, We will determine the Thevenin's Circuit Parameters (V_{OC} , I_{SC} , R_{th}) and plot the I-V characteristics of the following Circuit with respect to terminals **a**, **b**.

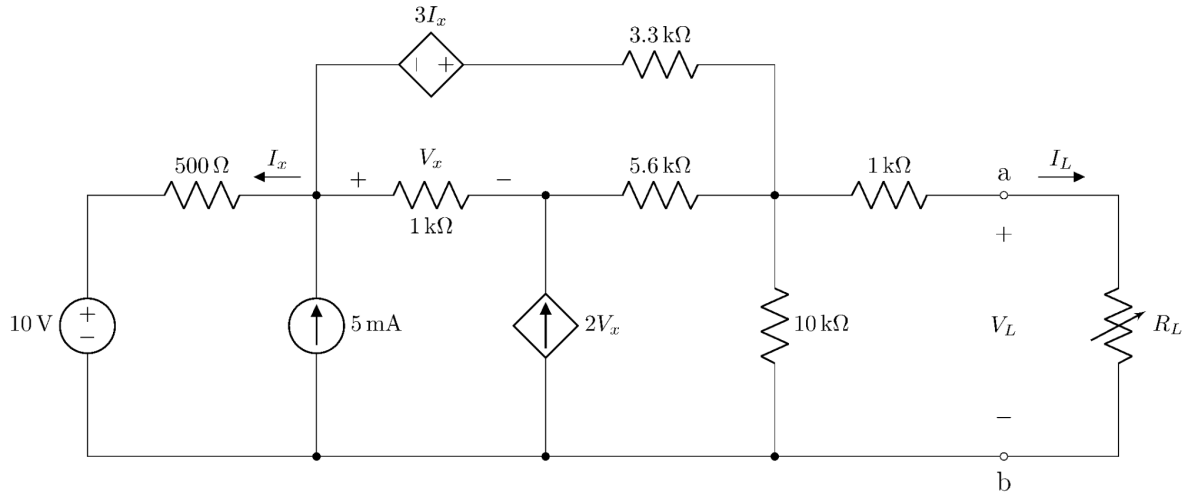

Circuit 4: Original Circuit

Step 1: Determining V_{OC}


Remove the load resistance R_L and find the open circuit voltage between terminals A & B. This voltage is called Thevenin's voltage, i.e., $V_{th}=V_{OC}$. It is also known as the Open Circuit Voltage.

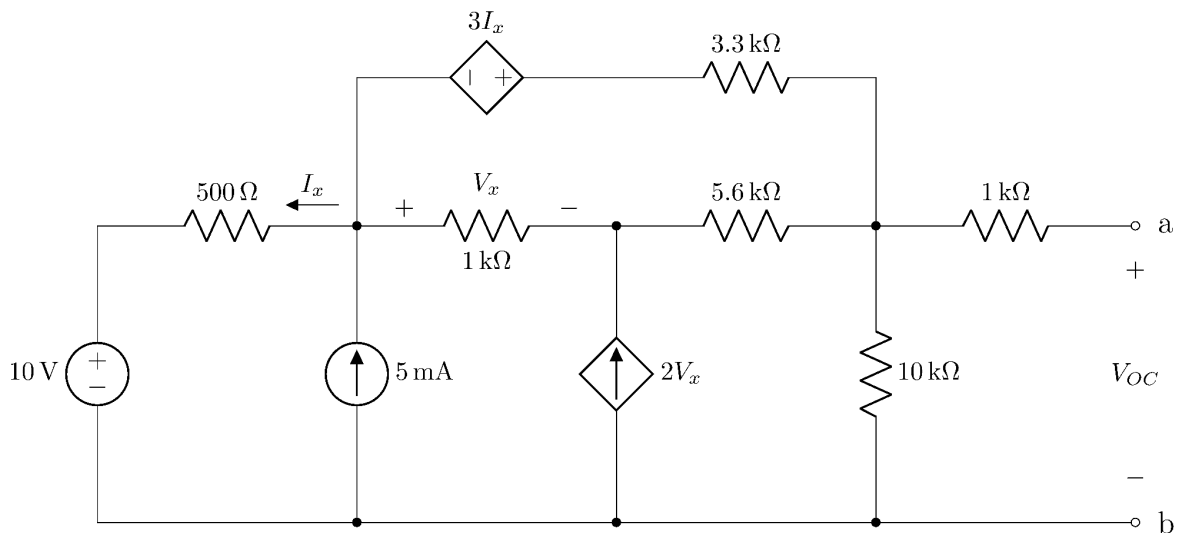

Circuit 5: Circuit for finding V_{OC}

Step 2: Determining I_{SC}

Place a short circuit between terminals A & B (simply connect them through a wire). The current through the short circuit is called Norton's Current, i.e., $I_N=I_{SC}$. It is also known as the Short Circuit Current.

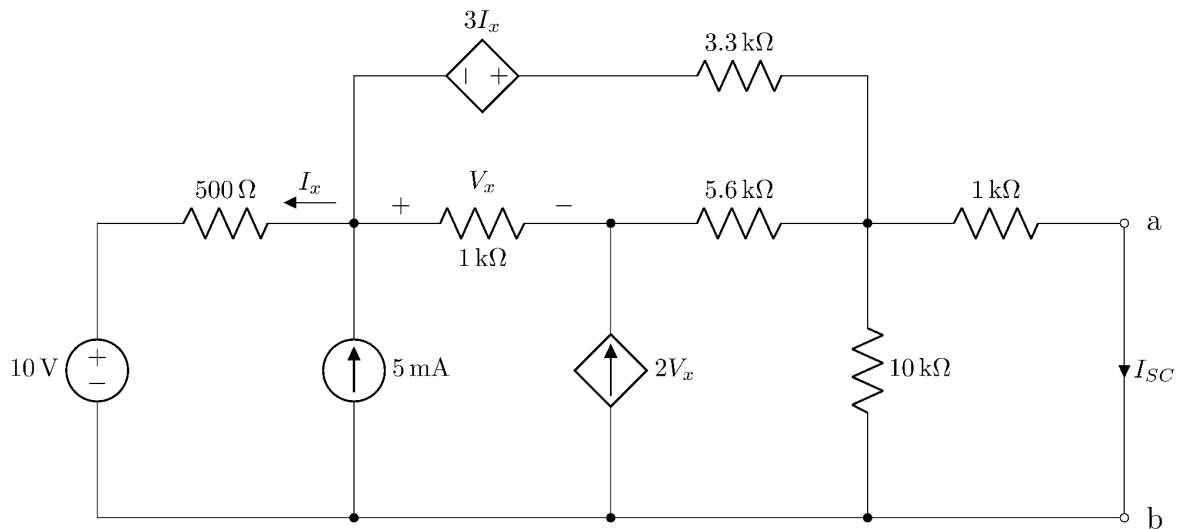

Circuit 6: Circuit for finding I_{sc}


Step 3: Determining R_{th}

Divide the Open Circuit Voltage by the Short Circuit Current to determine the Thevenin's Resistance.

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

Step 4: Constructing Thevenin's Equivalent Circuit

Construct Thevenin's equivalent circuit as shown in the following figure setting the voltage source at V_{th} volts and the series resistance at R_{th} ohms. The values shown here should closely match the corresponding values you determined from the earlier steps.

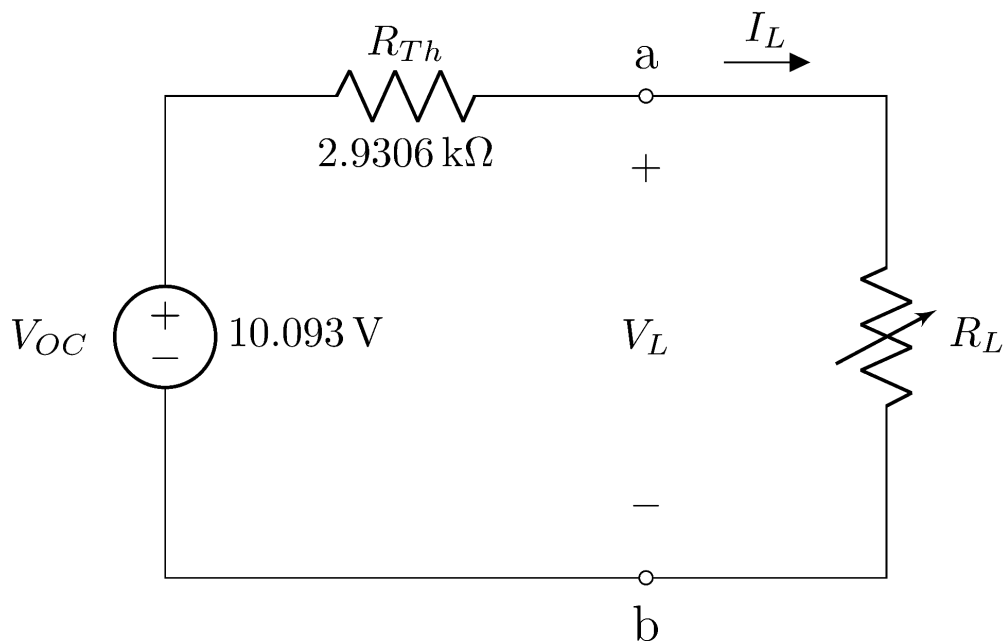


Circuit 7: Thevenin's Equivalent Circuit

Procedures

Finding V_{OC} using LTspice

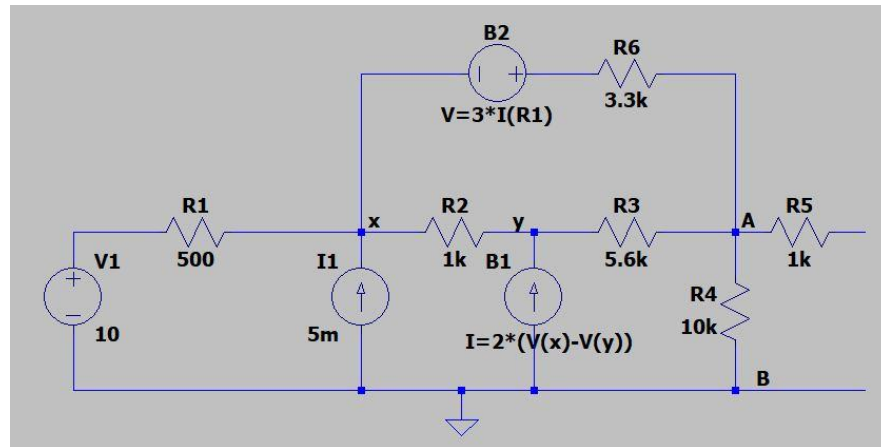- Draw **Circuit 5** in a new schematic. Modify the components with appropriate values and label the nodes.



- To measure open circuit voltage, V_{oc} , we have to run '**DC Operating Point**' analysis. To run the '**DC Operating Point**' analysis we have to write the analysis command. Find the '**Spice Directives**' option by **Right-clicking on the schematic** ☐ **Draft** ☐ **Spice Directives** or find it from the toolbar above.
- After clicking the '**Spice Directives**', the '**Edit Text on the Schematic**' window will appear. Now **Right-click on the blank space on this window** ☐ **Select 'Help me Edit'** ☐ **Analysis Command**. A window titled '**Edit Simulation Command**' will appear. Select '**DC op pnt**' ☐ **OK**. It will generate a '**.op**' command which is the command for DC operating point analysis. Place this command somewhere in the schematic.
- To run the simulation, click '**Run**'. Find the '**Run**' button from the above toolbar or **Right-click on the schematic** → **Run**.
- After clicking '**Run**' a new window titled '**Operating Point**' will appear, containing all node voltages and branch currents. From this window, note the voltage at node '**A**' (according to the circuit). This is the open circuit voltage, V_{oc} .


* D:\BRACU\CSE 250\Lab New\exp05\Draft1.asc

--- Operating Point ---


V(n002) :	10	voltage
V(x) :	12.1816	voltage
V(y) :	12.1814	voltage
V(a) :	10.0939	voltage
V(n001) :	12.1947	voltage
V(n003) :	10.0939	voltage
I(B2) :	-0.000636612	device_current
I(B1) :	0.000372589	device_current
I(I1) :	0.005	device_current
I(R5) :	0	device_current
I(R6) :	0.000636612	device_current
I(R4) :	-0.00100939	device_current
I(R3) :	-0.000372775	device_current
I(R2) :	1.86295e-007	device_current
I(R1) :	0.0043632	device_current
I(V1) :	0.0043632	device_current

Finding I_{SC} using LTspice

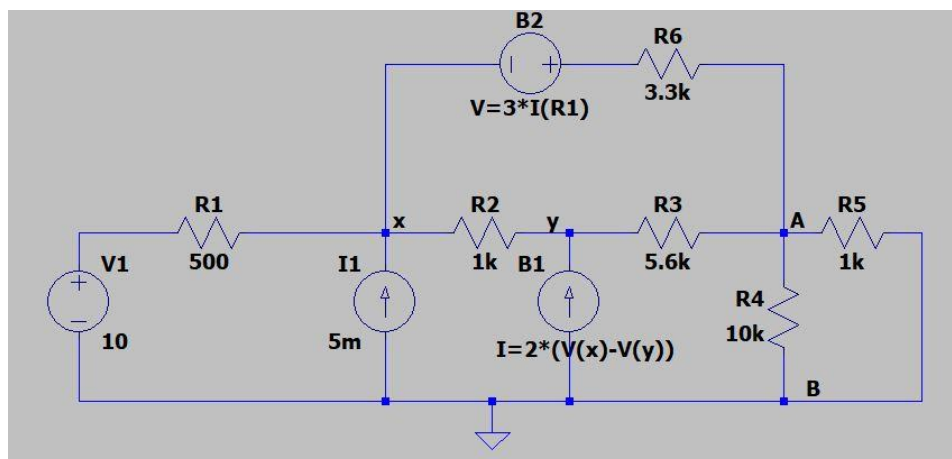- Draw **Circuit 6** in a new schematic. Modify the components with appropriate values and label the nodes.



- To measure the short circuit current I_{sc} , we have to run '**DC Operating Point**' analysis. Run the simulation in '**DC Operating Point**' analysis mode by following the steps mentioned earlier.
- After clicking '**Run**' a new window titled '**Operating Point**' will appear, containing all node voltages and branch currents. From this window, note the current through resistor **R5** (according to the circuit). This is the short circuit current, I_{sc} .

 * D:\BRACU\CSE 250\Lab New\exp05\Draft1.asc


--- Operating Point ---

V(n002) :	10	voltage
V(x) :	11.3071	voltage
V(y) :	11.3064	voltage
V(a) :	3.44448	voltage
V(n001) :	11.315	voltage
I(B2) :	-0.002385	device_current
I(B1) :	0.00140322	device_current
I(I1) :	0.005	device_current
I(R5) :	0.00344448	device_current
I(R6) :	0.002385	device_current
I(R4) :	-0.000344448	device_current
I(R3) :	-0.00140392	device_current
I(R2) :	7.01611e-007	device_current
I(R1) :	0.00261429	device_current
I(V1) :	0.00261429	device_current

To confirm the equivalency of the given circuit and its assessed Thevenin's equivalent circuit, we will compare their **I-V characteristics graphs**.

I-V Characteristics of the Given Circuit

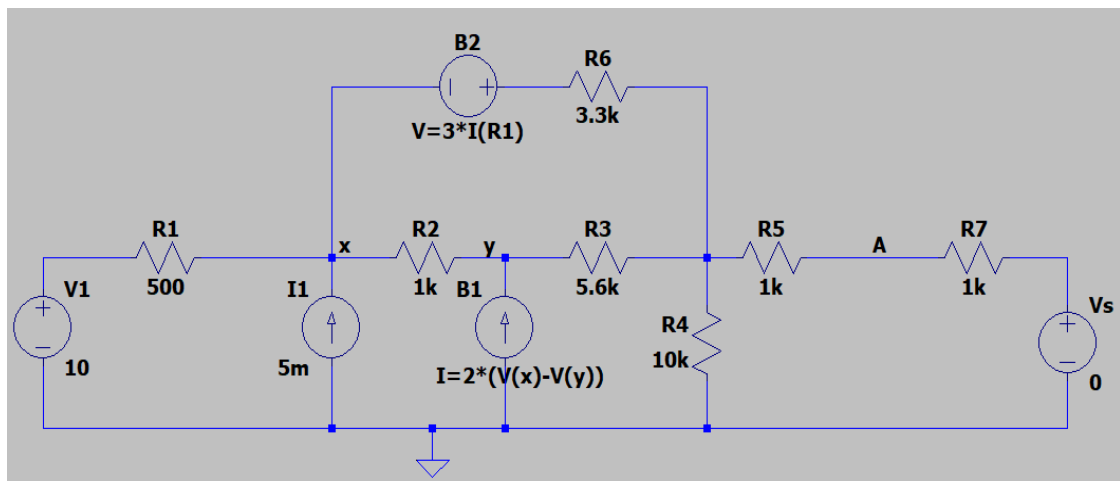
- Draw **Circuit 4** in a new schematic. Modify the components with appropriate values and label the nodes.



- Get the I-V characteristics graph by following the steps mentioned earlier. *[Hint: Run 'DC Sweep Analysis' simulation. In the graph, plot the voltage at node 'A', 'V(a)' (according to the circuit shown above, can be different in your case) in the X axis and the current through R7, 'I(R7)' (according to the circuit shown above).]*

I-V Characteristics of the Thevenin's Equivalent Circuit

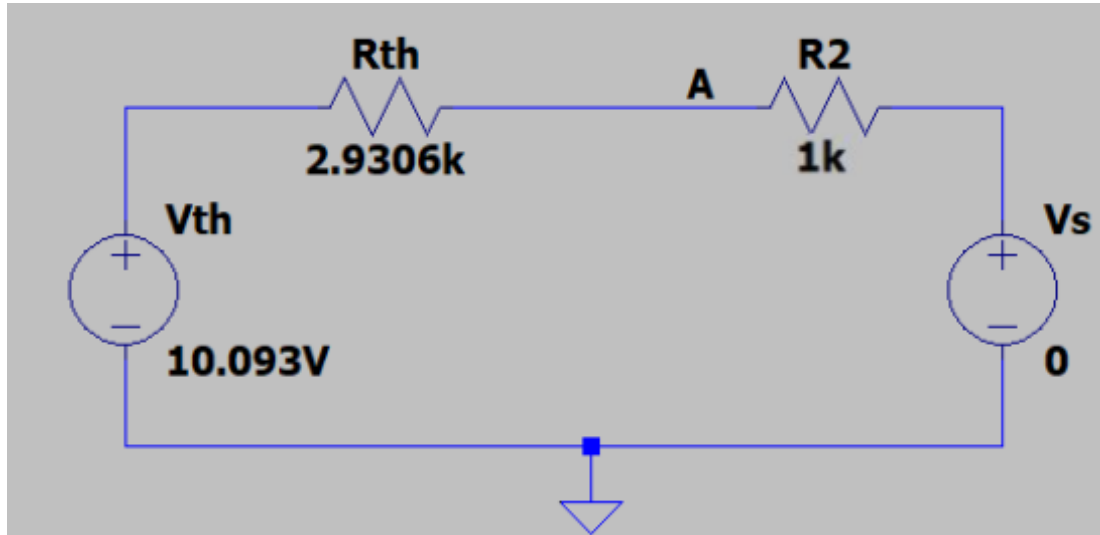- Draw **Circuit 7** in a new schematic. Modify the components with appropriate values and label the nodes. Notice that the value of the voltage source is equal to V_{th} and that of the resistance is equal to R_{th} .



- Get the I-V characteristics graph by following the steps mentioned earlier. *[Hint: Run 'DC Sweep Analysis' simulation. In the graph, plot the voltage at node 'A', ' $V(a)$ ' (according to the circuit shown above) in the X axis and the current through $R2$, ' $I(R2)$ ' (according to the circuit shown above).]*

Lab Work: Compare the I-V characteristics of **the Given Circuit & the Thevenin's Equivalent Circuit** and state your opinion on whether Thevenin's Theorem has been verified or not.


Part 2.2: Verification of Maximum Power Transfer Theorem using Software Simulation (LTSpice)

Objective

The aim of this experiment is to verify the Maximum Power Transfer theorem with reference to a given circuit using LTSpice. They will plot the Load Power of a given circuit against different values of Load Resistance using simulation and determine the Load Resistance Value for which the Maximum Load Power is achieved. They will also be able to verify the Maximum Power Transfer theorem using this information.

Theory

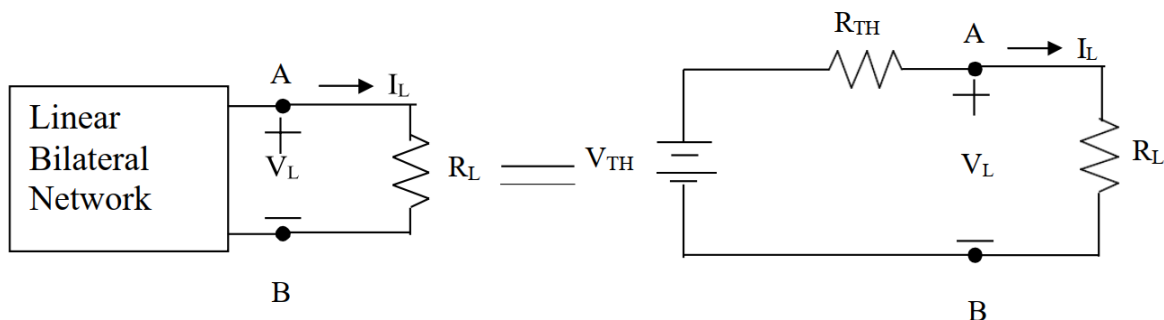The Maximum Power Transfer Theorem is a fundamental concept in electrical engineering that relates to the transfer of maximum power from a source to a load. The Maximum Power Transfer theorem states that *A resistive load will receive maximum power when its total resistive value is exactly equal to Thevenin's resistance of the network as "seen" by the load.*



We know that any circuit A terminated with a load R_L can be reduced to its Thevenin's equivalent. Now according to this theorem, the load R_L will receive maximum power when $R_L = R_{th}$. We can calculate the Maximum Power theoretically using the formula,


$$P_{\max} = \frac{V_{th}^2}{4R_{th}}$$

The theorem focuses on the transfer of power between a source and a load. In electrical circuits, power is transferred from a source (such as a generator) to a load (such as a resistor) through a transmission medium (such as wires or conductors).

It's worth noting that the Maximum Power Transfer Theorem is a theoretical concept and is not always practical or desirable in real-world scenarios. In many practical applications, impedance matching is employed to achieve efficient power transfer, but it may not always result in maximum power transfer. Design considerations, system constraints, and other factors often influence the choice of impedance matching in electrical circuits.

Procedures


We will use Thevenin's Equivalent Circuit we determined earlier to verify Maximum Power Transfer Theorem.

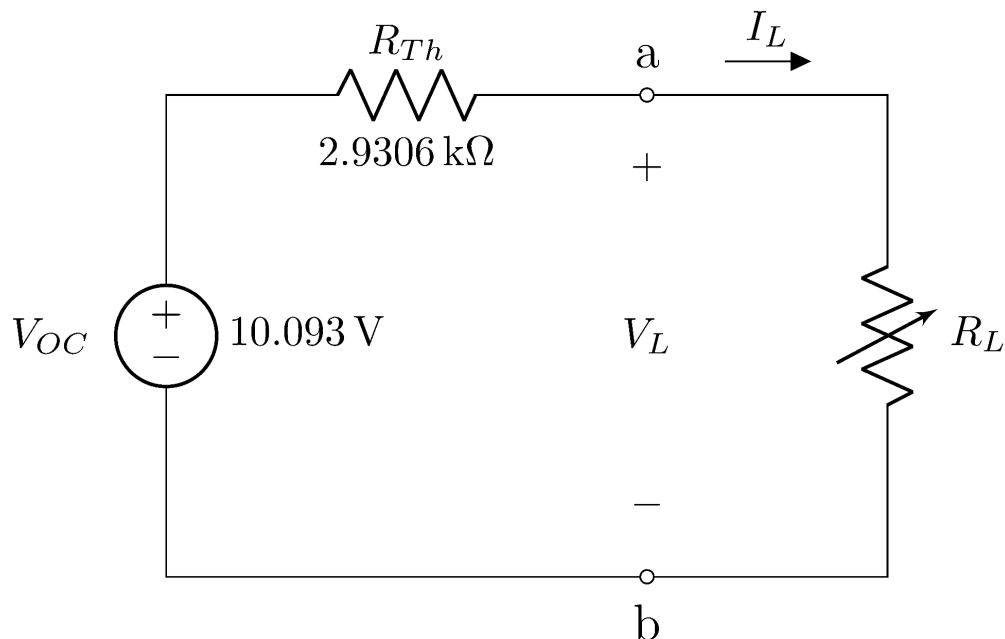


Circuit 7: Thevenin's Equivalent Circuit

Verifying Maximum Power Transfer Theorem using LTSpice

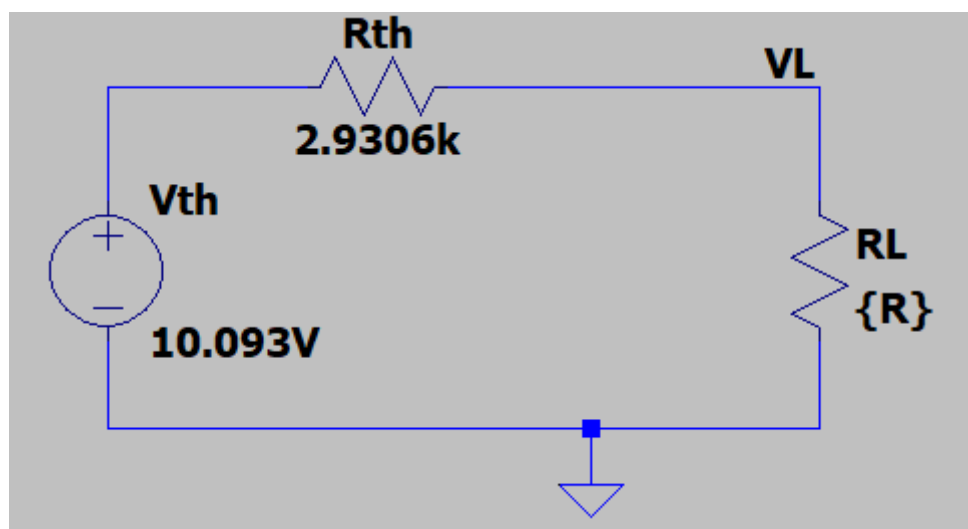- Draw the **Circuit 7** in a new schematic in LTSpice. Modify the components with their values and name the nodes. Notice that the value of the voltage source is equal to V_{th} and that of the resistance is equal to R_{th} .




- As we have to calculate the power at load resistance R_L for different values of R_L , we will vary the value of R_L . For this, set the value of R_L with $\{R\}$ so that R can be used as a variable parameter.
- To vary the value of R_L we have to do '*Parametric Sweep*' using the variable parameter R which we have set as the value of R_L . To do so, find the '*Spice Directives*' option by *Right-clicking on the schematic* ☐ *Draft* ☐ *Spice Directives* or find it from the toolbar above.
- After clicking the '*Spice Directives*', the '*Edit Text on the Schematic*' window will appear. Type '*.step param R 200 20k 100*' in the text box and click **OK**. It will generate a command. Place it somewhere in the schematic.

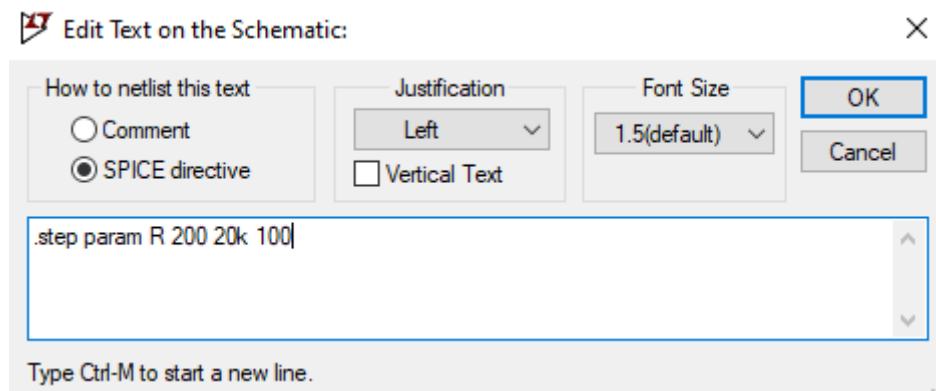


Notice the '**.step**' syntax here. This command causes an analysis to be repeatedly performed while stepping the temperature, a model parameter, a global parameter, or an independent source. Steps may be linear, logarithmic, or specified as a list of values. Here, '*.step param R 200 20k 100*' this command causes the parameter R to increase from $200\ \Omega$ to $20\ \text{k}\Omega$ with a step size 100 i.e. it will perform simulation for $R_L = 200\ \Omega, (200+100)\ \Omega, (200 + 2*100)\ \Omega \dots \text{up to } 20\ \text{k}\Omega$.

- To calculate the power at the load, we will measure the voltage and current at the load ($P_L = V_L * I_L$). To do so we have to do '**DC operating point**' analysis. Run the simulation in '*DC Operating Point*' analysis mode by following the steps mentioned earlier.
- To run the simulation, click '**Run**'. Find the '**Run**' button from the above toolbar or by just Right-clicking on the schematic.

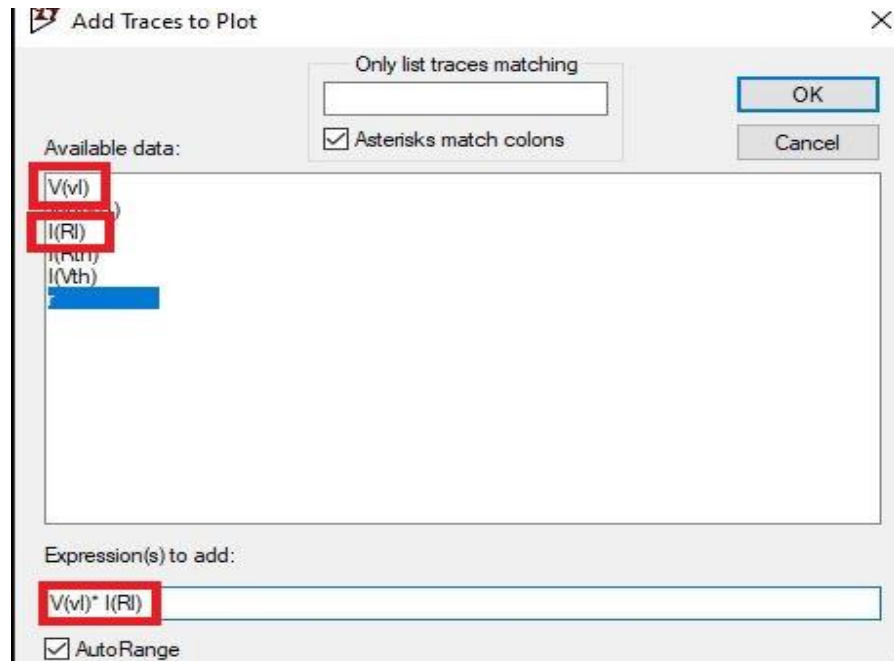- After the simulation 'run' is complete, a blank plot window will appear. *Now Right-click on the blank plot space* ☐ *Add trace* ☐ *Select V_L* ☐ *Type '*'* ☐ *Select $I(R_L)$* ☐ *OK*.



- A power vs resistance plot will be generated. On the Y axis, there is the power associated with the load resistance, and on the X axis, there are the values of load resistance R_L . Click on the title of the plot; a cursor will appear. Using this cursor, find the maximum power (peak of the graph) point from the plot and note down the corresponding value of the load resistance R_L from the X axis. The value should be equal to that of the Thevenin resistance.

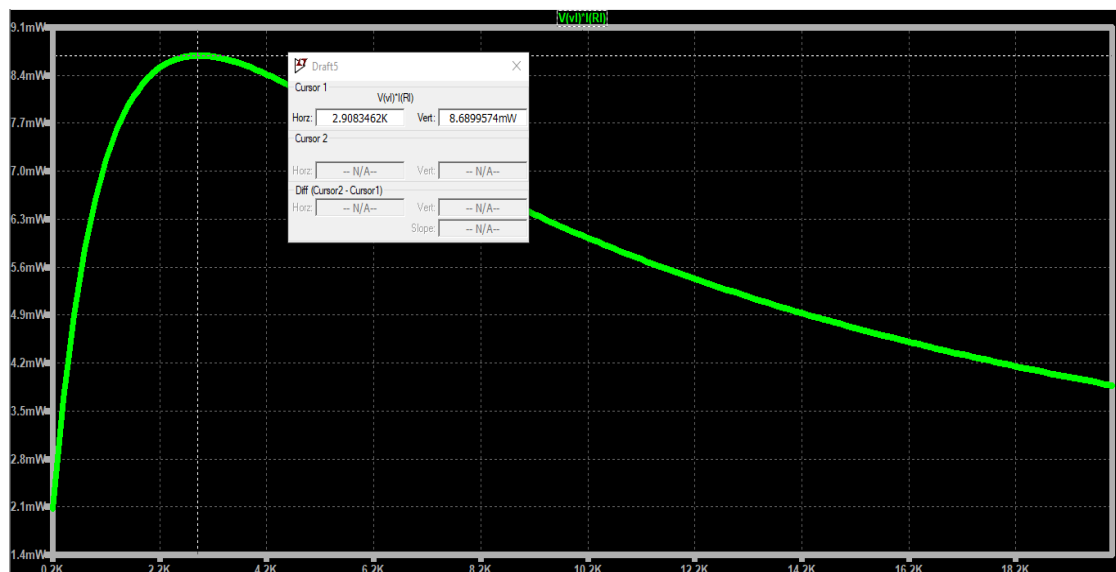

Lab Work: From the plot, Find out the value of R_L for which Maximum Power was achieved and state your opinion on whether Maximum Power Transfer Theorem has been verified or not.



Report

1. Answer to questions and Complete the Lab work sections.
 2. Save all your .asc and .plt files and make a zip file. You need to submit it with the report.
 3. Discussion [*comment on the obtained results and discrepancies*]. Start writing from below the line.
-